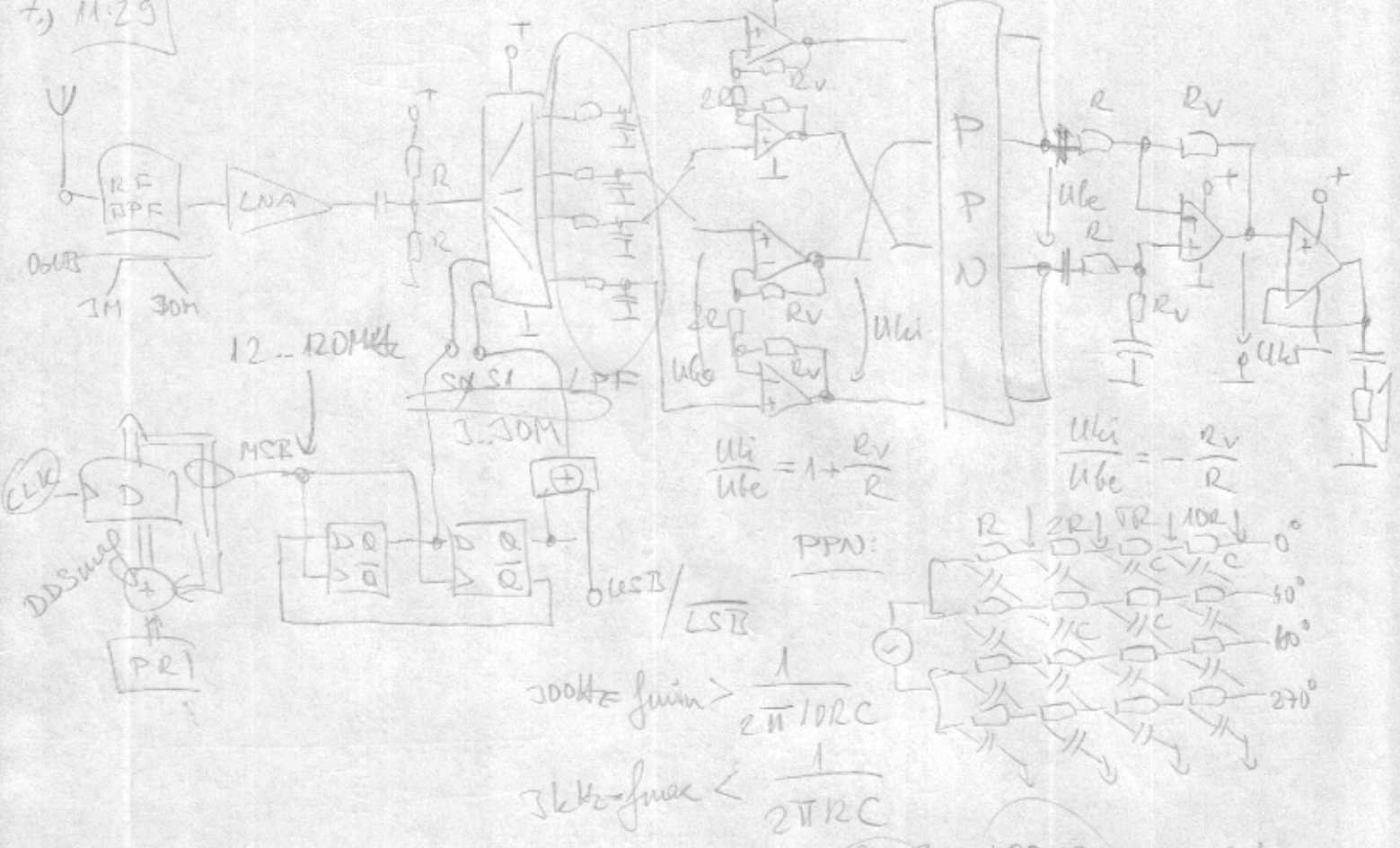


$1W @ 50\Omega \Rightarrow \frac{U^2}{50\Omega} = 1W \Rightarrow U = \sqrt{50} V$   
 $\sum_{in} P_{R_1} = \frac{U^2}{61,1\Omega} = \frac{50}{61,1} = 0,82W$   
 $P_{R_1} = \frac{(10U)^2}{61,1\Omega} = 82W$   
 $P_{R_2} = \frac{(10U - U)^2}{247,5\Omega} = 16,36W$

$P_{be} = 100W$   
 $P_{R_1} = 82W$   
 $P_{R_2} = 16,36W$   
 $\sum_{in} P_{R_1} = 0,82W$   
 $P_{ci} = 1W$   
 $\sum 100W$

7) 11:29



8) 11:28

