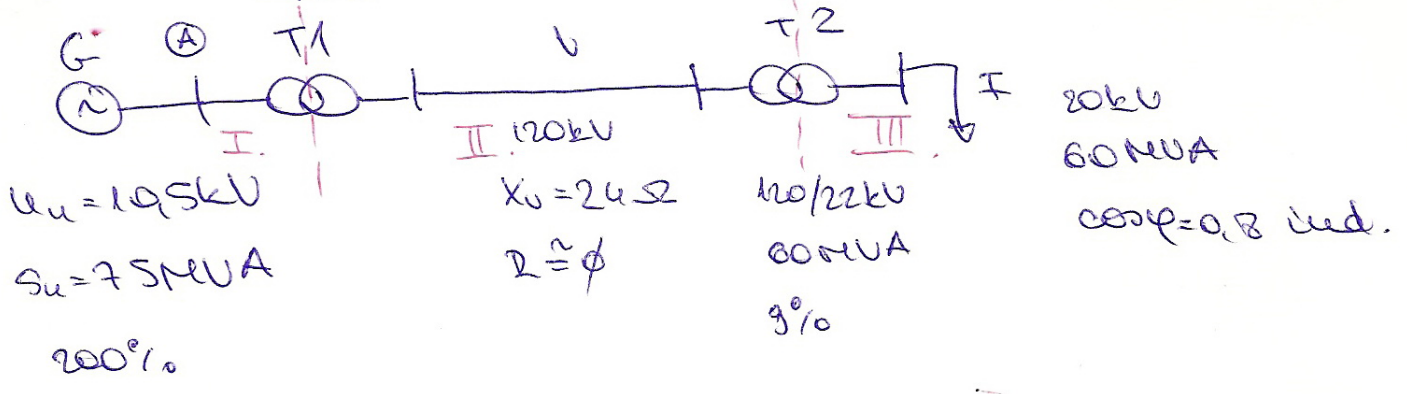



10% 70MVA 2009.03.24. Energetika 2016



Feltételezések :  $U_f = U_{FA}$

$U_g = ?$   
 $U^* = ?$   
 $I_g = ? \quad \frac{I_g}{I_{gu}} = ?$

	I	II	III	
$U_g$	$10,5 \cdot \frac{10}{12,6} = 8,65$	$20 \cdot \frac{120}{22} = 109,1$	20	kV vonali
$S_a$	60	60	60	MVA 3f
$Z_a$		$\frac{109,1^2}{60} = 198$		$\Omega$
$I_a$	$\frac{60}{\sqrt{3} \cdot 8,65}$			kA

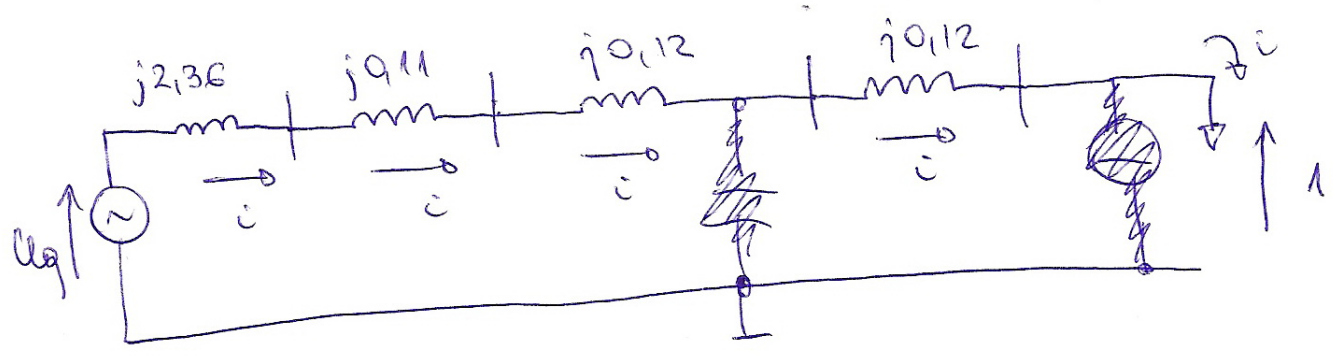

$$X_g = \frac{X_g}{Z_a^I} = \frac{\frac{X_g(\%) \cdot U_{gu}^2}{100}}{\frac{(U_a^I)^2}{S_a}} = \frac{X_g(\%)}{100} \frac{\left(\frac{U_{gu}}{U_a^I}\right)^2}{\frac{S_{gu}}{S_a}} =$$

$$= \frac{200}{100} \frac{\left(\frac{10,5}{8,65}\right)^2}{\frac{75}{60}} = 2,38$$

$$X_{T1} = \frac{X_{T1}^{(1)}}{Z_a^I} = \frac{X_{T1}^{(2)}}{Z_a^{II}} = \frac{\frac{\varepsilon}{100} \frac{(U_{T1u})^{(2)2}}{S_{T1u}}}{\frac{(U_a^{II})^2}{S_a}} = \frac{\varepsilon}{100} \frac{\left(\frac{U_{T1u}^{(2)}}{U_a^{II}}\right)^2}{\frac{S_{T1u}}{S_a}} =$$

$$= \frac{10}{100} \frac{\left(\frac{126}{109,1}\right)^2}{\frac{70}{60}} = 0,11$$

$$X_{T2} = \frac{9}{100} \frac{\left(\frac{120}{109,1}\right)^2}{\frac{60}{60}} = 0,12$$

$$X_U = \frac{X_U}{Z_a^{II}} = \frac{24}{198} = 0,12$$

~~\*\*\*~~

$$U_T = \frac{U_{T1u}}{U_a^{III}} = \frac{20}{20} = 1$$


induktiv

$$c = \frac{I_{T1u}}{I_a^{III}} = \frac{\frac{S_{T1u}}{\sqrt{3} U_{T1u}} (\cos\varphi - j \sin\varphi)}{\frac{S_a}{\sqrt{3} U_a^{III}}} = \frac{\frac{S_{T1u}}{S_a}}{\frac{U_{T1u}}{U_a^{III}}} (\cos\varphi - j \sin\varphi) =$$

$$= \frac{\frac{60}{60}}{\frac{20}{20}} (0,8 - j0,6) = 0,8 - j0,6$$

$$U_{qg} = U_{\pm} + i j (X_q + X_{T1} + X_U + X_{T2}) =$$
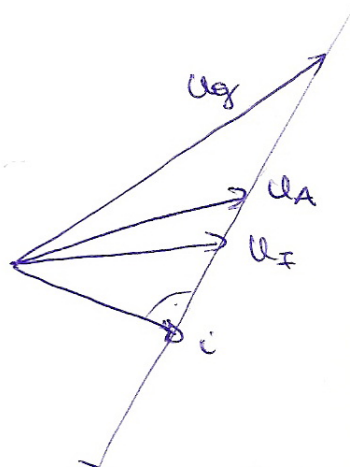
$$= 1 + (0,8 - j0,6) j 2,71 = 2,63 + j2,17 = 3,4 \angle 39,5^\circ$$



$$U^A = U_{\pm} + i j (X_{T1} + X_U + X_{T2}) = 1 + (0,8 - j0,6) j (0,35) =$$

$$= 1,21 + j0,88 = 1,24 \angle 13^\circ$$

$$|U_{\pm}^A| = U^A U_{qg}^I = 1,24 \cdot 8,65 / \sqrt{3} = 6,19 \text{ kV}$$

$$U_v^A = U_{\pm}^A \sqrt{3} = 10,7 \text{ kV}$$

$$\left( \frac{U_v^A}{U_{qgn}} \right) \cdot 100 \approx 102 \%$$

$$U_f^B = U^B U_{af}^I$$

$$|i_q| = 1 \quad I_q = i_q I_a^I = 4 \text{ kA}$$

$$I_{gn} = \frac{75}{\sqrt{3} \cdot 10,5} = 6,12 \text{ kA} = \frac{9 \text{ pu}}{\sqrt{3} U_{qgn}}$$

$$\frac{I_q}{I_{gn}} \cdot 100 = 97 \%$$

$$|i_v| = 1 \quad I_v = i_v I_a^I$$

$$I_A = U_A \cdot i_A^* = (1,21 + j0,22) \cdot 1,24 e^{j13} \cdot 1 e^{j\varphi} = 0,8 + j0,9$$


$$S_A = I_A S_{a3\varphi} = (0,8 + j0,95) 60 = 48 + j57 \text{ MVA}$$

$$I_F = U_F i_F^* = 1 \cdot 1 e^{j\varphi} = 0,8 + j0,6$$

$$S_{F3\varphi} = 48 + j36 \text{ MVA}$$

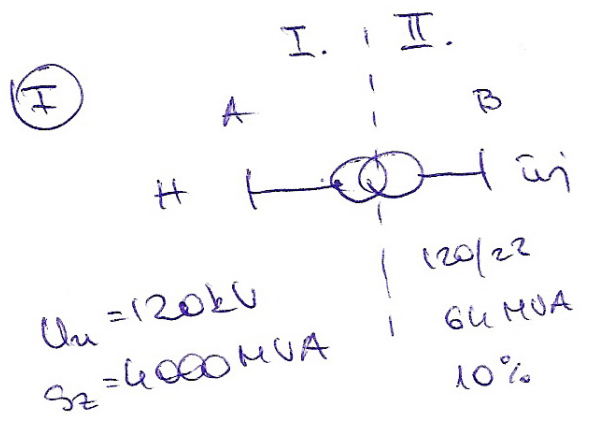57-36 = 21 Mvar 2 trafo & vezeték

$$q_A - q_F = 10^2 (X_{T1} + X_{T2} + X_U) = 0,35$$




	I	II	
$U_a$	120	22	kV
$S_a$	64	64	MVA
$I_a$	0,308	1,38	kA

$$U_H = 120 \text{ kV}$$

$$S_2 = 6000 \text{ MVA}$$


$$S_2^B = ?$$

$$I_2^B = ?$$

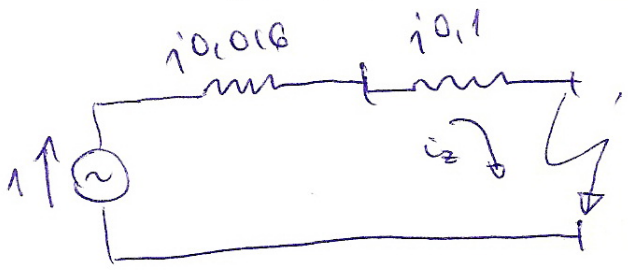

$$X^H (\Omega) = \frac{U_H^2}{S_2}$$
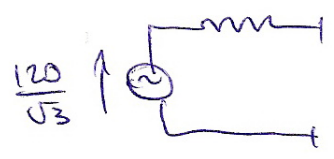
$$X^H = \frac{\left(\frac{U_H^H}{U_a^I}\right)^2}{\frac{S_2}{S_a}} = 0,016$$



$$X^T = 0,1$$

$$U^H = \frac{U_F^H}{U_a^I} = \frac{U_U^H}{U_a^I}$$

$$|i_2| = \frac{U_H}{\sqrt{(X_H + X_T)^2}} = \frac{1}{0,016 + 0,1} = 8,62$$


$$I_2^B = i_2 I_a^B = 14,5 \text{ kA}$$

$$S_2^B = U_{pu}^B \cdot I_2^B = 1 \cdot 8,62 = 8,62$$

$$S_2^B = 8,62 \cdot 64 = 552 \text{ MVA}$$

$$S_{23f}^B = \sqrt{3} U_u^B I_2^B = \sqrt{3} \cdot 22 \cdot 14,5 \text{ kA} = 552 \text{ MVA}$$

$\infty$  kebalokan

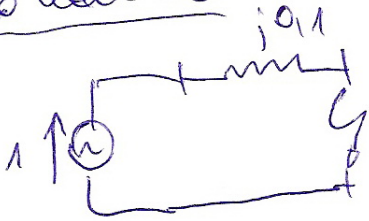

$$|i_2| = 10 = \frac{1}{0,1}$$

$$S_2 = 1 \cdot 10 = 10$$


$$S_2 = 10 \cdot 64 = 640 \text{ MVA}$$

↓  
transformator  
sangat adrihati  
teherikuelnye



$$U_u = 22 \text{ kV}$$

$$S_2 = 552 \text{ MVA}$$

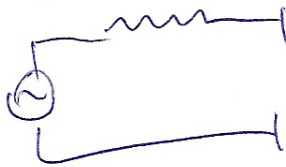

$$X_{\text{cred}}^B = X_H + X_{tr} = \frac{U_u^B^2}{S_2^B} = \frac{U_u^H^2}{S_2^H} + \frac{e}{100} \frac{U_u^2}{S_{tr}}$$

$$\frac{1}{S_2^B} = \frac{1}{S_2^H} + \frac{1}{S_2^{tr}}$$

$$S_2^{tr} = \frac{S_{trn}}{\frac{e}{100}} = 6,4$$