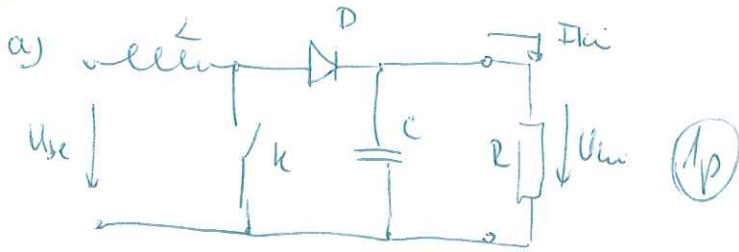




2) Boost,  $U_{bc} = 150V$ ,  $U_{hi} = 300V$ ,  $I_{ki} = 10A$ ,  $\Delta I_L = 10A$ ,  $\Delta U_{hi} = 1V$ ,  $f = 40kHz$



b)  $d = 1 - \frac{U_{bc}}{U_{hi}} = 1 - \frac{150}{300} = 0,5$  (1p)

$t_{be} = d \cdot T = 0,5 \cdot 25\mu s = 12,5\mu s$  (1p)

$L \geq \frac{U_{bc} \cdot t_{be}}{\Delta I_L} = \frac{150 \cdot 12,5\mu s}{10A} = 187,5\mu H$  (2p)

$C \geq \frac{I_{ki} \cdot t_{be}}{\Delta U_{hi}} = \frac{10A \cdot 12,5\mu s}{1V} = 125\mu F$  (2p)

c) 
$$\left. \begin{aligned} I_C &= I_D - I_{ki} \\ I_C &= I_D - I_{ki} \end{aligned} \right\} \Rightarrow \hat{I}_D = \hat{I}_L = \frac{1}{1-d} I_{ki} + \frac{\Delta I_L}{2} = 25A$$
 (1p)

$\hat{I}_C = 25A - 10A = 15A$  @ 40kHz


d)  $\hat{I}_L = \hat{I}_D = \hat{I}_L = I_{ki} + \frac{\Delta I_L}{2} = \frac{1}{1-d} I_{ki} + \frac{\Delta I_L}{2} = 25A$  (1p)

e)  $\hat{U}_k = \hat{U}_D = U_{hi} = 300V$  (1p)

f)  $I_{k_{eff}} = \frac{U_{bc} \cdot T}{2L} d(1-d) = \frac{150V \cdot 25\mu s}{2 \cdot 187,5 \cdot 10^{-6}} \cdot 0,5(1-0,5) = \frac{\Delta I_L}{2} = 2,5A$  (1p)

$\leq 10p$

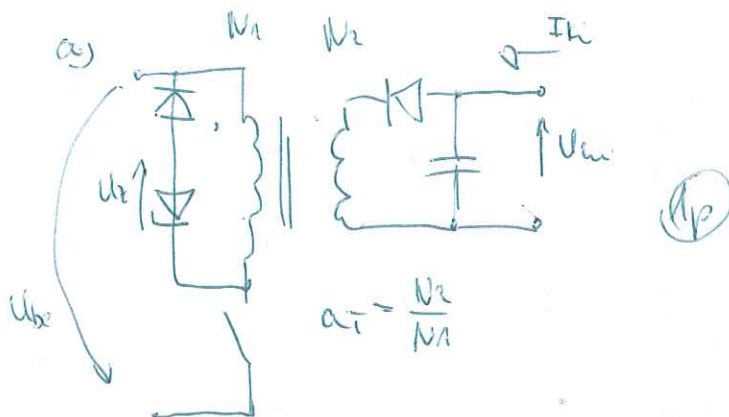3) Flyback,  $U_{bc} = 325V$ ,  $U_{hi} = 24V$ ,  $a_T = 0,2$ ,  $f = 50kHz$ ,  $P_{ki} = 120W$



b)  $d = \frac{U_{hi}}{a_T \cdot U_{bc} + U_{hi}} = \frac{24}{0,2 \cdot 325 + 24} = 0,269$  (0,5p)

$t_{be} = d \cdot T = 0,269 \cdot 20\mu s \approx 5,4\mu s$  (0,5p)

0,15

$$L_{\mu} \geq \frac{U_{be} \cdot I_{be}}{\Delta I_L} = \frac{325 \cdot 5,4 \mu\text{s}}{2A} = \underline{877,5 \mu\text{H}} \quad (2p)$$

$$c) C \geq \frac{I_{Lk} \cdot \Delta t_{be}}{\Delta U_{Lk}} = \frac{5A \cdot 5,4 \mu\text{s}}{0,2V} = \underline{135 \mu\text{F}} \quad (2p)$$

$$d) \underline{I_{k}^n} = \underline{I_{Lk}^n} = I_{Lk} \cdot A_T + \frac{\Delta I_L}{2} = \frac{1}{1-d} I_{k1} + \frac{\Delta I_L}{2} = \frac{1}{1-0,269} \cdot 5A \cdot 0,2 + \frac{2}{2} = \underline{2,136A} \quad (1p)$$

$$\underline{I_D^n} = \frac{I_{Lk}^n}{A_T} = \frac{2,136}{0,2} \approx \underline{11,18A} \quad (1p)$$

$$e) \underline{U_{Lmax}} = U_{be} + U_{Lk}^n = 325 + \frac{24}{0,2} = \underline{445V} \quad (1p)$$

$$\underline{U_{Dmax}} = U_{be}^n + U_{Lk} = 0,2 \cdot 325 + 24 = \underline{89V} \quad (1p)$$

$$f) \underline{U_{Lmin}} = U_{Lk}^n = 24/0,2 = \underline{120V} \quad (1p)$$

Σ 11p

Route 1's:

0 - 14 : (1)

15 - 20 : (2)

21 - 25 : (3)

26 - 30 : (4)

31 - 35 : (5)